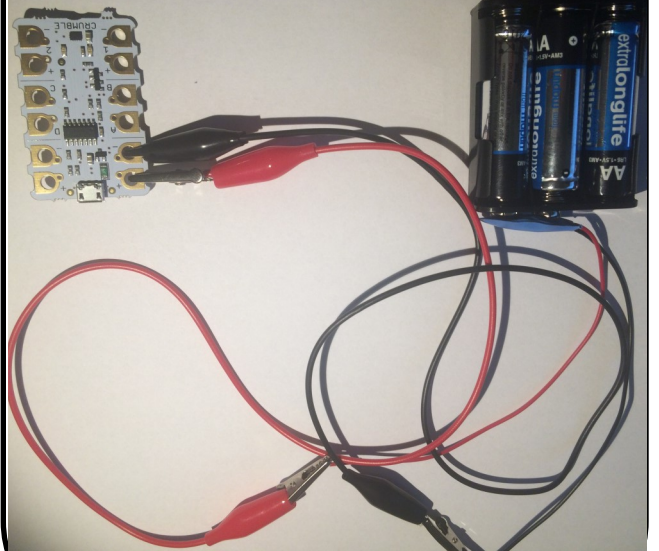


Batteries totalling between 4.5v and 5v max should be used to power motors, sparkles, lights etc
 Not everything needs battery power
 Make sure positive connects to positive and wires are not crossed over as this can damage components



Wiring


Hints

Make sure the positive wire is not touching the negative wire or the batteries will heat up a short circuit will occur and nothing will work.

The colour of the wire will not affect how it works but many people like to use the red and black wires to remind them that they are power wires.

A simple switch could be used to turn the crumble on and off by breaking or connecting one of the power wires.

Crumble Maker Cards Power

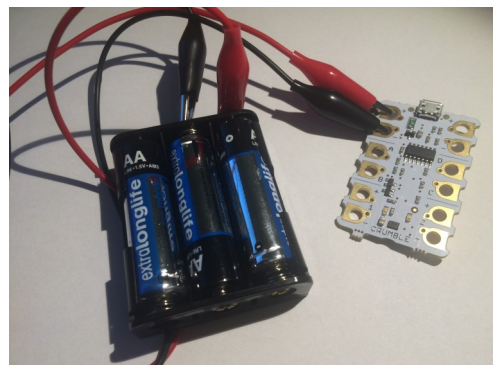

This work is licensed under the Creative Commons Attribution-NonCommercial 3.0 Unported License. To view a copy of this license, visit <http://creativecommons.org/licenses/by-nc/3.0/> or send a letter to Creative Commons, 444 Castro Street, Suite 900, Mountain View, California, 94041, USA.